


**Variable Resistor:** A resistor whose resistance can be deliberately changed.  
 Also called: potentiometer

7. What are some common uses for a variable resistor?

Volume Knobs, dimmer switches

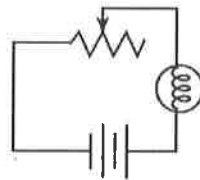
8. If the resistance in the circuit is increased, what will happen to the brightness of the lamp? Why?

$I = \frac{V}{R}$  If R is increased, then "I" or the current will decrease + light will dim.



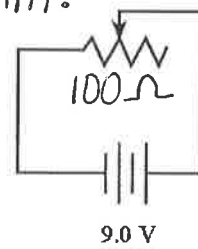9. If the resistor is set to 100 ohms, what is the current in the circuit?

$$I = \frac{V}{R} = \frac{9.0V}{100\Omega} = 0.09A$$



**Electrical Power and Energy**

**Power:** rate at which energy is used

**Mechanical Power**

$$P = \frac{W}{t} = \frac{\vec{F} \cdot \vec{d}}{t} = \vec{F} \cdot \vec{v}$$

Units:  $\left[ \frac{J}{s} \right]$   
 $\downarrow$   
 watt  $[W]$

$$P = \frac{E}{t}$$

**Electrical**

Units:  $\left[ \frac{J}{s} \right] = [W] \text{ watt}$

$$\frac{PE_e}{t} = P = IV$$

$\downarrow \quad \downarrow$

$$\left[ \frac{C}{t} \right] \left[ \frac{PE_e}{C} \right] \quad \left[ \frac{C}{s} \right] \left[ \frac{J}{C} \right]$$

**Electrical Power**

$P = IV$

$P = I(IR) = I^2R$  units = Watts  $[W]$

$V = IR$

**Electrical Energy**

$PE_e = P \cdot t$

$W = P \cdot t$   
work

$P = \left( \frac{V}{R} \right) V = \frac{V^2}{R}$

Units: Joules  $[J]$

1. A mini light bulb is connected to a 1.5 volt battery and draws a current of 28 mA.

a) How much power does it dissipate?  $P = IV = (0.028A)(1.5V) = 0.042W$

b) How much energy does the light bulb use in 1.0 minute?

$PE_e = P \cdot t = (0.042 \frac{J}{s}) \left( \frac{60s}{min} \right) = \frac{2.5J}{min}$

Use "g" =  $\frac{10\text{m}}{\text{s}^2}$

2. Refer to the drawing of a motor lifting a brick.

$P = IV$


a) How fast can the motor raise a 2.0 kg brick?

$$P = F \cdot \vec{v} \quad \vec{v} = \frac{IV}{F} = \frac{(1.5\text{A})(12\text{V})}{20\text{N}} = 0.90 \frac{\text{m}}{\text{s}}$$

$$IV = F \cdot \vec{v} \quad F = ma$$

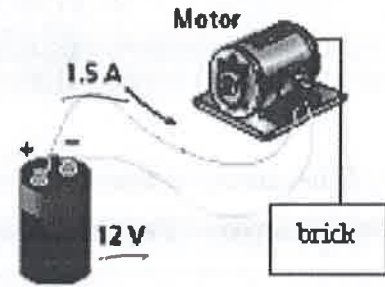
b) How much energy will the motor use in 10.0 seconds?

$$PE_e = P \cdot t = (IV) \cdot t = (1.5\text{A})(12\text{V})(10.0\text{s}) = 180\text{J}$$




A battery runs a motor that lifts a brick.

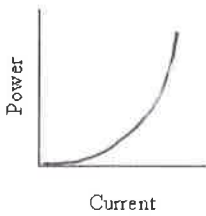3. Sketch each of the following relationships:




$P = I^2 R$

Control: R

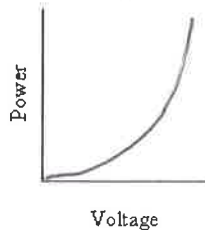


$P = \frac{V^2}{R}$

Control: R

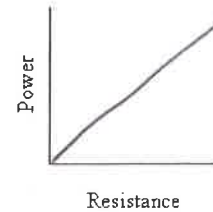


Control: I  $P = I^2 R$

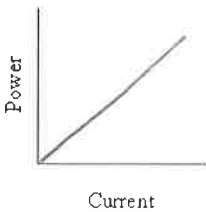


$P = IV$

Control: V

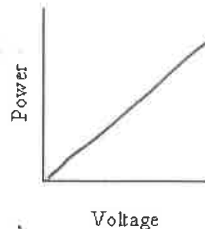

$P = IV$

Control: I

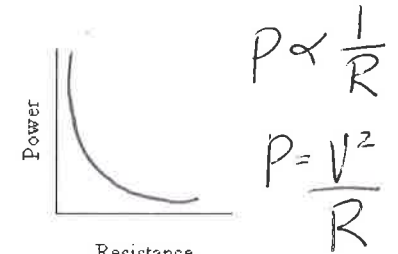

Control: V  $P \propto \frac{1}{R}$   
 $P = \frac{V^2}{R}$

4. If the resistance of an appliance attached to a constant source of voltage is doubled, how much power does it now dissipate?


$$P = \frac{V^2}{R} \quad \frac{V^2}{(2R)} = \left(\frac{1}{2}\right)P$$

$$2R = \frac{1}{2} \text{ Power}$$

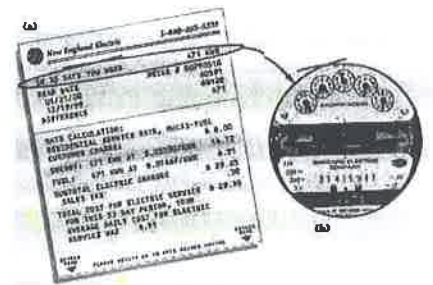5. The electric meter connected to a house is marked "kilowatthours." The electric bill lists a charge to the homeowner for using 471 KWH (kWh) for the month.

What is being measured in kilowatthours? **Energy**

(1000 watts)(1hr) = P · t = measure of energy



$PE_e = P \cdot t$

**ENERGY!** Kilowatt-hour (kWhr): The amount of energy used running 1000 watts for one hour.

6. How many joules of energy are equivalent to one kilowatt-hour?

$$1000\text{W} = 1000 \frac{\text{J}}{\text{s}} \quad 1000 \frac{\text{J}}{\text{s}} \cdot 3600\text{s} = 3.6 \times 10^6 \text{J} \quad 1\text{hr} = 3600\text{s}$$

$\text{Kwhr} = 3.6 \times 10^6 \text{J}$

7. Determine the energy cost for the consumer whose bill is shown above.

$\$0.0355 \text{ / kWhr} \cdot 471 \text{ kWhr} = \$16.72$  conversion factor  $\frac{1 \text{ kWhr}}{3.6 \times 10^6 \text{ J}}$