
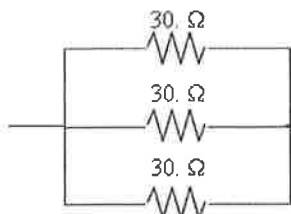


Have ready by class on Tuesday 6/4.

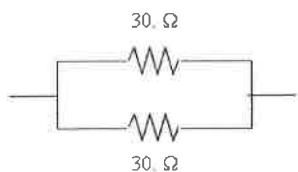7. Calculate the equivalent resistance of each resistor segment below.

Shortcut for identical parallel resistors:




$$R_{eq} = \left( \frac{1}{30\Omega} + \frac{1}{30\Omega} \right)^{-1} = \left( \frac{1}{15\Omega} \right)^{-1} = \left( \frac{1}{R_T} \right)^{-1} = 15\Omega$$

$$R_{eq} = \left( \frac{1}{30\Omega} + \frac{1}{30\Omega} + \frac{1}{30\Omega} \right)^{-1} = 10\Omega$$

Equivalent resistance is the resistance of one divided by # of resistors in circuit.

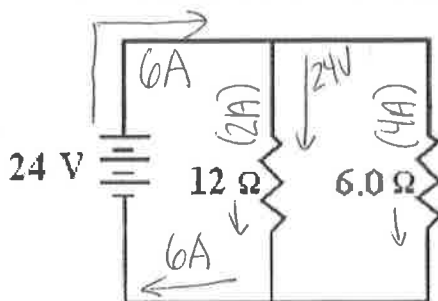8. Calculate the voltage drop across each resistor and the current through each resistor. Calculate the total current in the circuit and the equivalent resistance of the circuit.




$$R_{eq} = \left( \frac{1}{12\Omega} + \frac{1}{6\Omega} \right)^{-1} \quad R_{eq} = 4\Omega = R_T$$


$$I_T = \frac{V_T}{R_T} = \frac{24V}{4\Omega} = 6A$$

$$V_T = I_T R_T$$

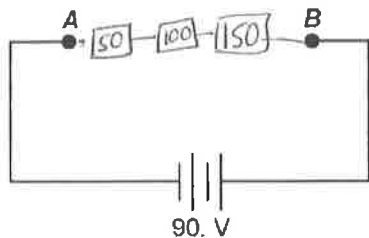9. A 50.  $\Omega$ , a 100.  $\Omega$  and a 150.  $\Omega$  resistor are to be connected in the circuit below between A and B. What type of connection will have the highest resistance? The lowest resistance? Complete each circuit and calculate each current.



highest  $R_T$

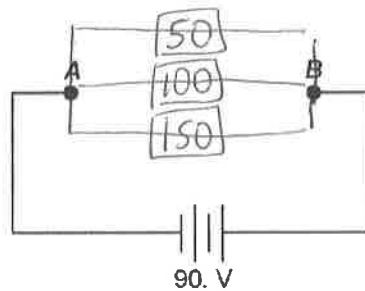

lowest  $R_T$


$$R_T = 300\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{90.V}{300\Omega} = \boxed{0.30A}$$

$$R_{eq} = \left( \frac{1}{50\Omega} + \frac{1}{100\Omega} + \frac{1}{150\Omega} \right)^{-1} = 27\Omega$$

$$I_T = \frac{90.V}{27\Omega} = \boxed{3.3A}$$

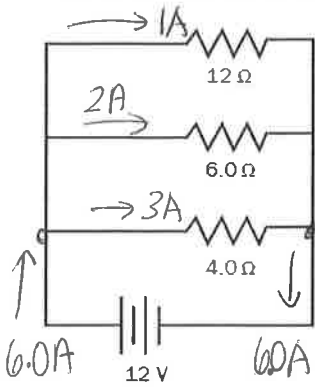10. Calculate the voltage drop across each resistor and the current through each resistor. Calculate the total current in the circuit and the equivalent resistance of the circuit.




R	I	V
12Ω	1.0A	12V
6.0Ω	2.0A	12V
4.0Ω	3.0A	12V

$V = IR$


$R_{eq} = 2\Omega \quad V_T = 12V \quad I_T = 6.0A$

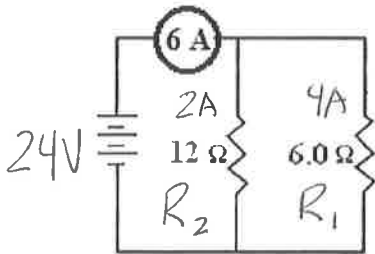11. Determine the current through each resistor by using a proportion.




$\frac{R_2}{R_1} = \frac{I_1}{I_2} \quad \frac{12\Omega}{6.0\Omega} = \frac{4.0A}{2.0A}$   
 2:1 ratio

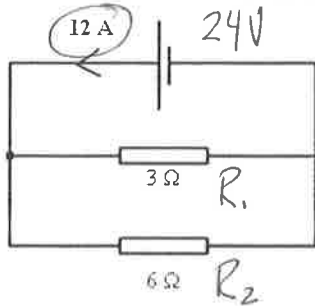12. Determine the current through each resistor in the circuits below using a proportion.



$\frac{R_1}{R_2} = \frac{I_2}{I_1}$

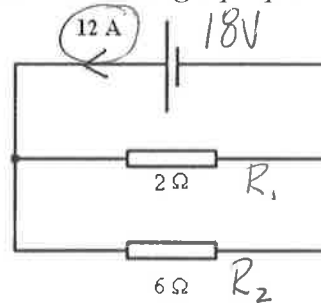


1:2 ratio  $\frac{3\Omega}{6\Omega} = \frac{4A}{8A}$

1:3 ratio  $\frac{2\Omega}{6\Omega} = \frac{3A}{9A}$

13. A 12Ω heater, a 20Ω hair dryer, and a 25Ω toaster are connected in parallel to a 120. volt power source. Sketch an appropriate schematic. Include a meter capable of measuring the total current and a meter capable of measuring the voltage drop across the heater. Find the reading on each meter.


$I_T =$   
 $V_T =$   
 $R_{eq} =$

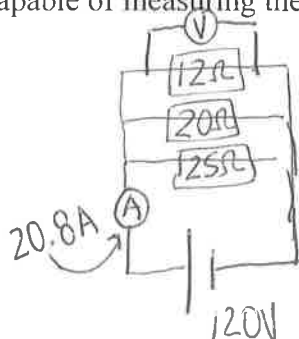

$V_T = 120V$   
 $R_{eq} = 5.77\Omega$   
 $I_T = \frac{120V}{5.77\Omega} = 20.8A$   
 $V_{drop} \text{ across } 12\Omega = 120V$

**Junction:** place where two or more wires meet in a circuit

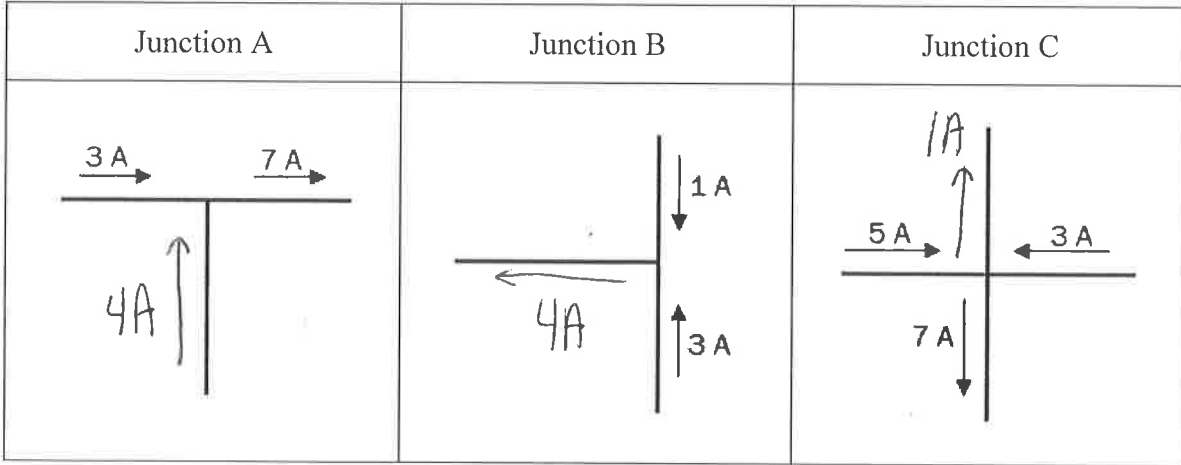- Determine the magnitude and direction of the current in the unlabeled wire.




**Kirchhoff's First Law (Current Law, Junction Rule):**



The total current directed into a junction must equal the total current directed out of the junction.

NOTE:


conservation of charge principle

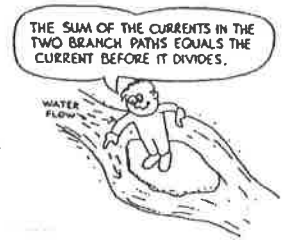

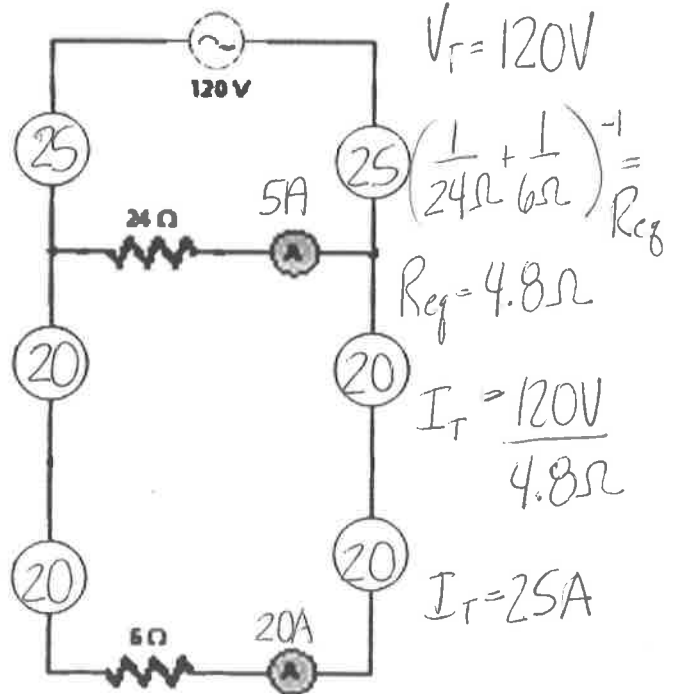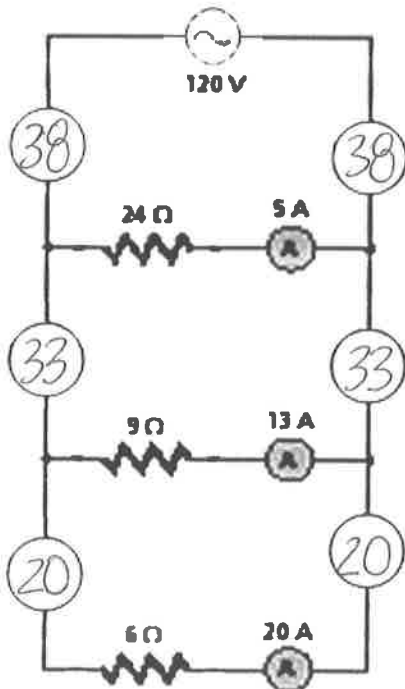- Determine the reading on each blank ammeter.
- Determine the new readings now that the 9 Ω resistor is removed.




Parallel Connection

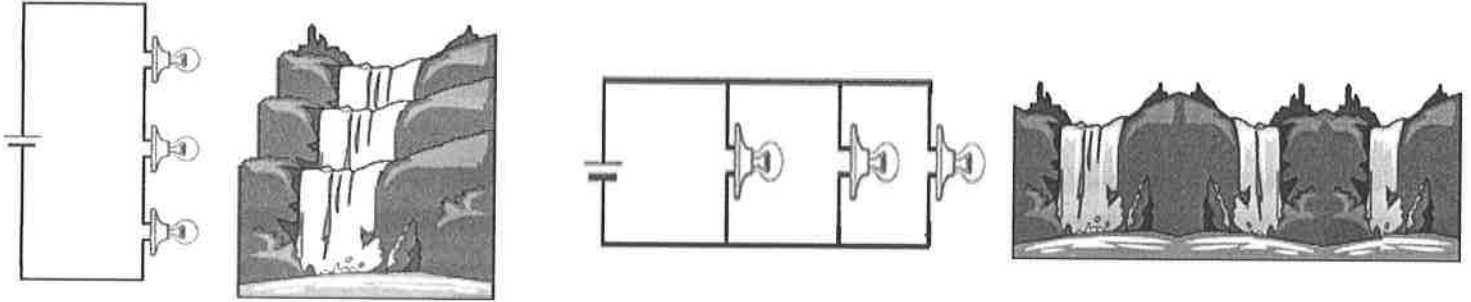


Characteristic	Series Circuit	Parallel Circuit
Number of pathways for current	one	multiple
Current	same	sum of all the pathways
Potential Difference (Voltage)	sum of all the drops	same
Overall resistance	sum of $R$ (high)	sum of $\frac{1}{R_T}$ (low)
Power	low	high

Influencing the Flow Rate on a Tollway

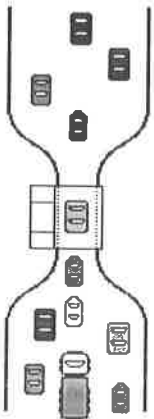

A Single Resistor

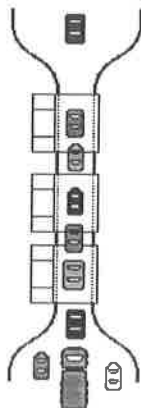

Three Resistors Placed in Series




Three Resistors Placed in Parallel
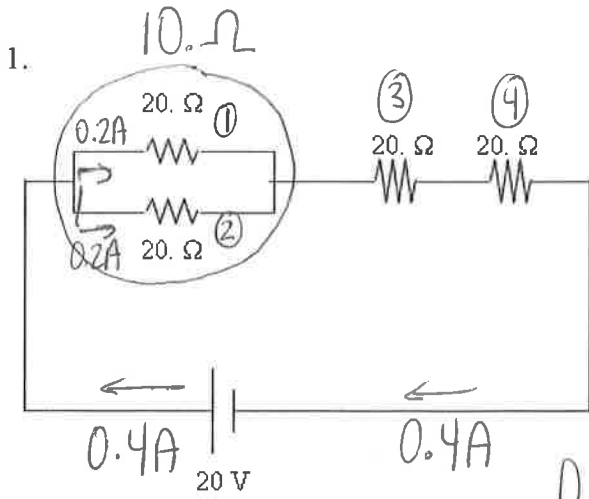
# Combination Circuits

IB 11

In each circuit below, determine the voltage drop across each resistor and the current through each resistor.




$$R_T = 50. \Omega$$


$$V_T = 20V$$

$$I_T = \frac{20V}{50. \Omega} = 0.4A$$

R	V	I
1) 20.Ω	4V	0.2A
2) 20.Ω	4V	0.2A
3) 20.Ω	8V	0.4A
4) 20.Ω	8V	0.4A

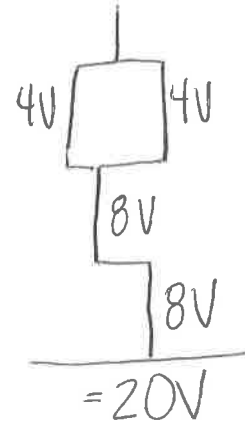

2.

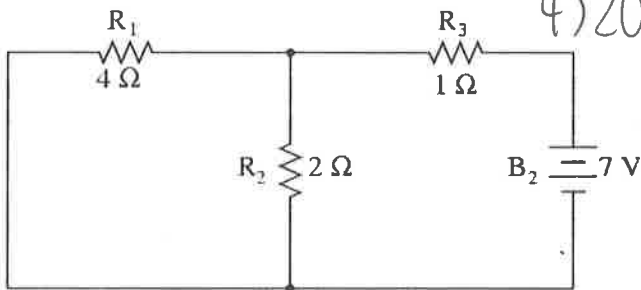

3.

