



## Mini-Circuit Lab

- 1) Create a series circuit with two bulbs.  
Draw a schematic of circuit.  
\* Get initials from Ms. Rosenthal.



- 2) Create a parallel circuit with two bulbs.  
Draw a schematic of the circuit.  
\* Get initials from Ms. Rosenthal.

