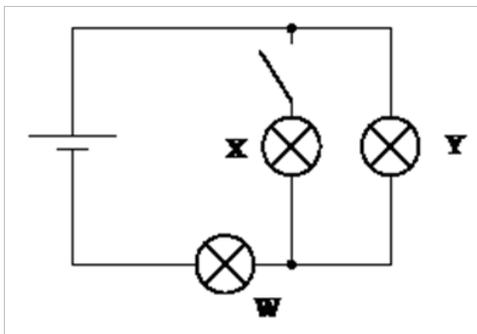


5. Three identical filament lamps (assume constant resistance) are connected to a source of emf as shown.


Predict what will happen when the switch is closed.




### Circuits with Multiple Emfs

I. Emfs in series in the same direction: **add the voltages**

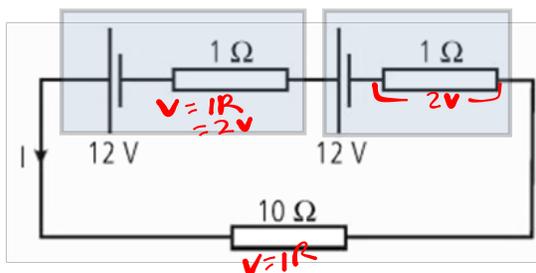
1. Determine the current in the following circuit.



2A

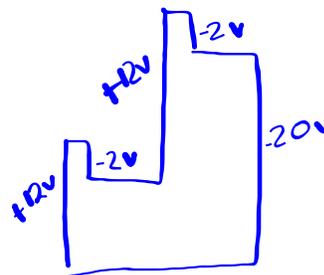

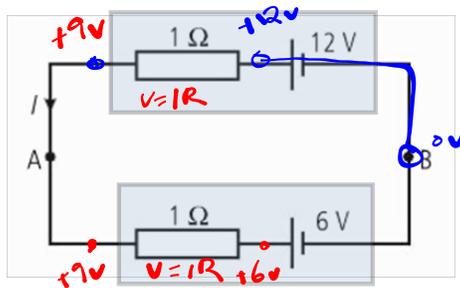- II. Emfs in series in opposite directions: **subtract the voltages**  
 2. Determine the current in the following circuit.




$$I = \frac{V}{R} = \frac{(+12\text{V} - 6\text{V})}{2\ \Omega} = \underline{3\text{A}}$$


Application of series emfs in opposite directions: **recharging a secondary cell**

Direction of current flow: **backwards through the secondary cell**

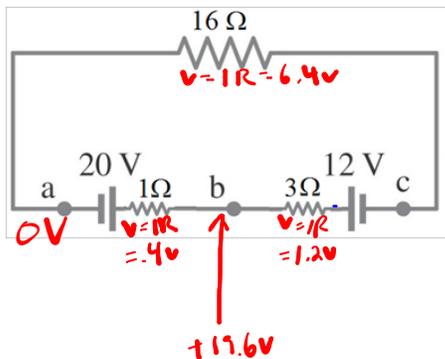3. Determine the current in the following circuit. Which is the primary cell and which is the secondary cell?





$$I = 4\text{A}$$

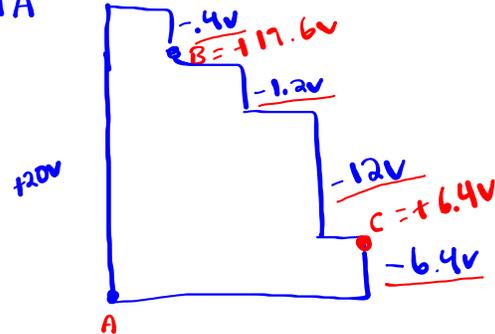

III. EMFs in parallel: **same EMF but add internal resistances**

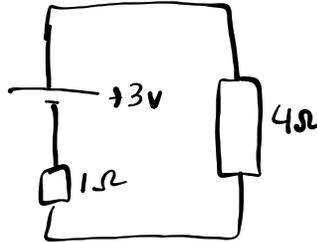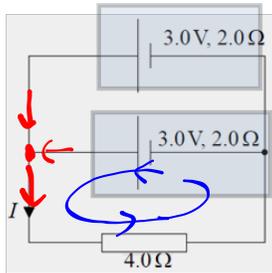4. Determine the current in the following circuit. Each identical cell has an emf of 3.0 V and an internal resistance of 2.0 ohms.



$$I = \frac{V}{R} = \frac{3V}{5\Omega} = .6A$$

### Kirchoff's Circuit Laws

**Loop Rule:** Around any closed loop in a circuit, the sum of the EMFs equals the sum of the potential differences. (total voltage rises = total voltage drops)

Conservation of . . .energy


**Formula:**  $\Sigma V = 0$

**Junction Rule:** At any junction in a circuit, the sum of the currents entering the junction equals the sum of the currents leaving the junction. (total current in = total current out)

Conservation of . . .electric charge

**Formula:**  $\Sigma I = 0$

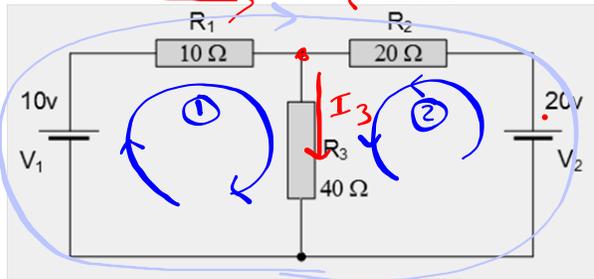1. Determine the current through resistor  $R_3$ .



$$\begin{bmatrix} I_1 & I_2 & I_3 & \\ 10 & 0 & 40 & 10 \\ 0 & 20 & 40 & 20 \\ 1 & 1 & -1 & 0 \end{bmatrix}$$

$$I_1 = -.143A$$

$$I_2 = .429A$$

$$I_3 = .286A$$

Loop 1

$$+10v - I_1 \cdot 10\Omega - I_3 \cdot 40\Omega = 0$$

Loop 2

$$+20v - I_2 \cdot 20\Omega - I_3 \cdot 40\Omega = 0$$



Junction

$$I_1 + I_2 = I_3$$

$$1 - I_1 - 4(I_1 + I_2) = 0$$

$$1 - I_2 - 2(I_1 + I_2) = 0$$

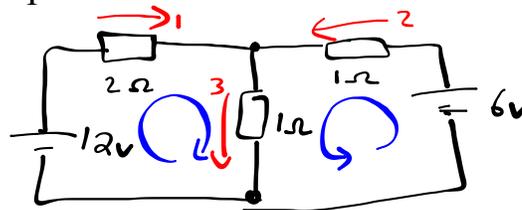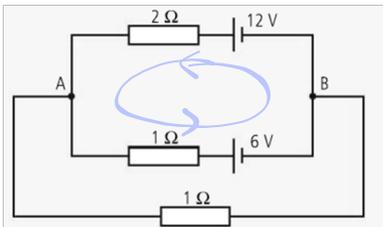2. Determine the currents in the following circuit as well as the potential difference between points A and B.



Redraw to look like circuit in Example #1

$$12 - 2I_1 - I_3 = 0$$

$$6 - I_2 - I_3 = 0$$

$$I_1 + I_2 = I_3$$

$$I_1 = 3.6A$$

$$I_2 = 1.2A$$

$$I_3 = 4.8A$$


### Internal Resistance of Cells

**Electromotive force (emf):** total energy per unit charge supplied around a circuit by the cell

**Terminal Voltage ( $V_{\text{term}}$ ):** potential difference across the terminals of the cell

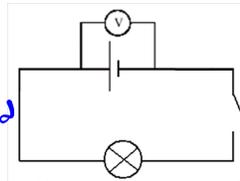1. Compare the terminal voltage of the cell when the switch is open to the terminal voltage when it is closed.

$$V_{\text{term open}} > V_{\text{closed}}$$



2. Compare the emf of the cell to its terminal voltage when the switch is:
  - a) open
  - b) closed

$$\begin{array}{ll} \text{a) open} & \text{b) closed} \\ \mathcal{E} = V_{\text{Term}} & \mathcal{E} > V_{\text{Term}} \end{array}$$

3. Explain these observations.

**Internal resistance (r):** the resistance supplied by the materials within the cell

think of a cell as . . . a perfect emf and a small resistor.

Mathematical model:



$$\mathcal{E} = I R_T$$

$$\mathcal{E} = I (R + r)$$

$$\mathcal{E} = IR + Ir$$

$\underbrace{\quad}_{V_{\text{Term}}}$

$$V_{\text{Term}} = -rI + \mathcal{E}$$

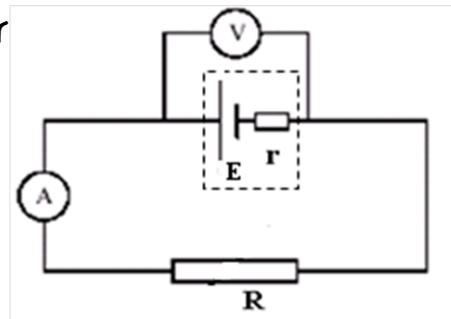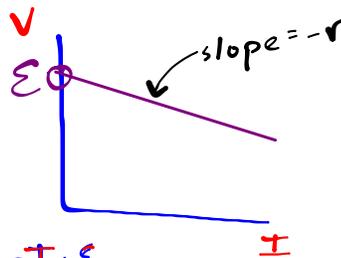

4. Use the math model to make some inferences about the behavior of a circuit containing a cell with internal resistance.

a)  $\text{Emf} = V_{\text{term}} \dots$  **open circ. voltage**  
 when no current is flowing (when  $R$  is infinite or open circuit) or if it is an ideal cell ( $r = 0$ )

b) When  $R \gg r \dots$   $\text{emf} = IR + Ir$      $\text{emf} \approx IR$      $\text{emf} \approx V_{\text{term}}$

c) When  $R = 0 \dots$   $\text{emf} = Ir$      $I = \text{emf}/r$      $I = I_{\text{max}}$   
**short circuit current**

5. A resistor is connected to a 12 V source and a switch. With the switch open, a voltmeter reads the potential difference across the battery as 12 V yet with the switch closed, the voltmeter reads only 9.6 V and an ammeter reads 0.40 A for the current through the resistor. Calculate the internal resistance of the source and the maximum possible current.

$$\mathcal{E} = IR_T = IR + Ir$$

$$\mathcal{E} = V_{\text{term}} + Ir$$


$\uparrow$      $\uparrow$      $\uparrow$   
 12V    9.6V    .4A

$$r = \frac{2.4\text{V}}{.4\text{A}} = 6\Omega$$

$$I_{\text{max}} \quad R = 0$$

$$I = \frac{\mathcal{E}}{r} = \frac{12\text{V}}{6\Omega} = 2\text{A}$$

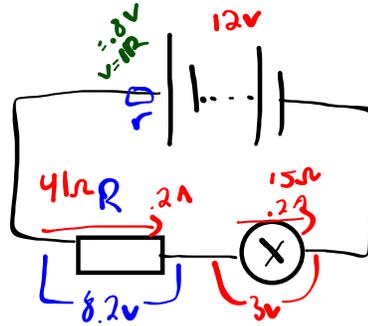6. A resistor  $R$  and a filament lamp  $L$  are connected in series with a battery. The battery has an emf of  $12\text{ V}$  and internal resistance  $4.0\ \Omega$ . The potential difference across the filament of the lamp is  $3.0\text{ V}$  and the current in the filament is  $0.20\text{ A}$ . Determine the resistance  $R$ .



**Resistance:** ratio of potential difference applied across a piece of material to the current through the material

**Ohm's Law:** for a conductor at constant temperature, the current flowing through it is proportional to the potential difference across it over a wide range of potential differences

Relationship:



Georg Simon Ohm  
(1787 – 1854)