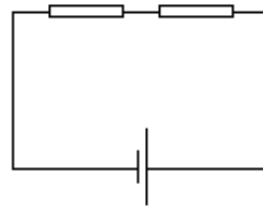


11. In which direction should current flow in order to recharge a secondary cell? Why?

Backwards through the cell – from positive to negative to reverse the chemical reaction within the cell

### Series Circuits



Current	same everywhere	$I_T = I_1 = I_2 = \dots$
Voltage	split up	$V_T = V_1 + V_2 + \dots$
Resistance	adds up	$R_T = R_1 + R_2 + \dots$
Power (brightness)	adds up	$P_T = P_1 + P_2 + \dots$


Ratios:  $\frac{P_1}{P_2} = \frac{V_1}{V_2} = \frac{R_1}{R_2}$  Control:  $I_1 = I_2$

1. Determine the current through and the voltage drop across each resistor in the circuit below.


$$R_T = 6\Omega + 3\Omega = 9\Omega$$

$$I_T = V_T / R_T = 18\text{V} / 9\Omega = 2\text{A} = I_6 = I_3$$

I	V
3Ω 2A	6V
6Ω 2A	12V

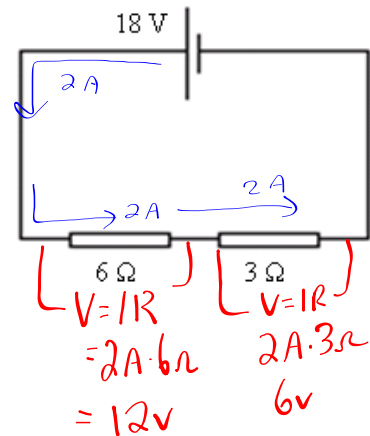


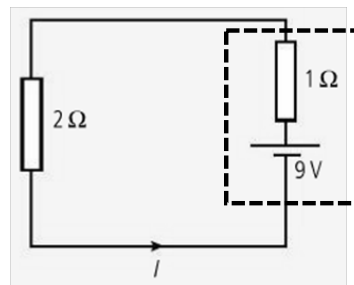2. A battery with an emf of 9 V and an internal resistance of 1 ohm is connected to a 2-ohm resistor as shown. How much current is in the circuit and what is the terminal potential difference?




**Potential Divider:** Resistors in series act as a “potential (voltage) divider.” They split the potential of the source between them.

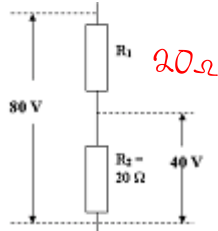
3. A  $20\Omega$  device requires  $40\text{ V}$  to operate properly but no  $40\text{ V}$  source is available. In each case below, determine the value of added resistor  $R_1$  that will reduce the voltage of the source to the necessary  $40\text{V}$  for device  $R_2$ .




(A)

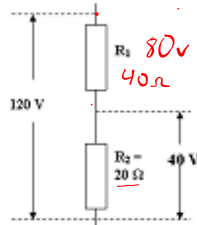

(B)

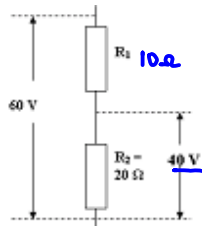


(C)

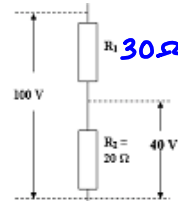

(D)

**Parallel Circuits**

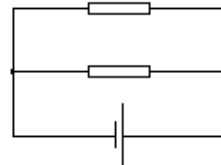

Current	split up	$I_T = I_1 + I_2 + \dots$
Voltage	same everywhere	$V_T = V_1 = V_2 = \dots$
Resistance	adds down	$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$
Power (brightness)	adds up	$P_T = P_1 + P_2 + \dots$


Ratios:  $\frac{P_1}{P_2} = \frac{I_1 V}{I_2 V} = \frac{I_1}{I_2} = \frac{V/R_1}{V/R_2} = \frac{R_2}{R_1}$  Control:  $V_1 = V_2$

4. Determine the current through and the voltage drop across each resistor in the circuit below.

$$R_{eq} = \left( \frac{1}{6\Omega} + \frac{1}{3\Omega} \right)^{-1} = 2\Omega$$

$$I = V/R = \frac{24V}{2\Omega} = 12A$$

	I	V
3Ω	8A	24V
6Ω	4A	24V


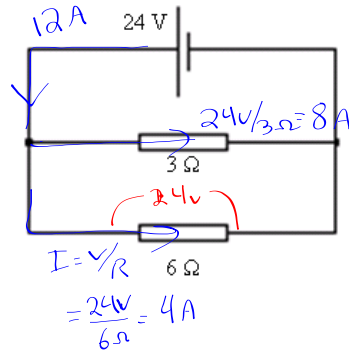


5. A cell with an emf of 6 volts and an internal resistance of 1 ohm is connected as shown. Determine the total current in the circuit and the terminal potential difference.

$$R_T = 1\Omega + 2\Omega$$

$$I_T = V/R = \frac{6V}{3\Omega} = 2A$$


	I	V
1Ω	2A	2V
4Ω	1A	4V
4Ω	1A	4V

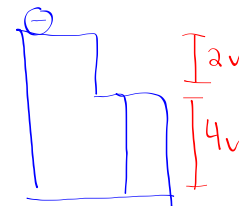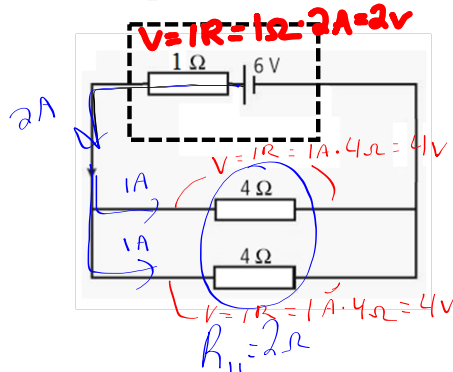

**Ammeter:** measures current

Placement: in series


Ideal ammeter: zero resistance

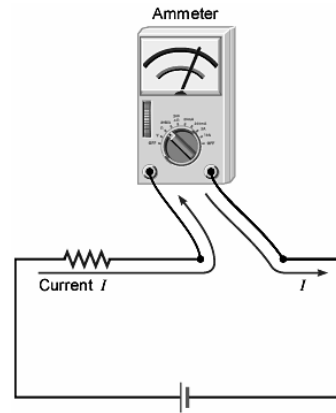



**Voltmeter:** measures potential difference

Placement: parallel

Ideal voltmeter: infinite

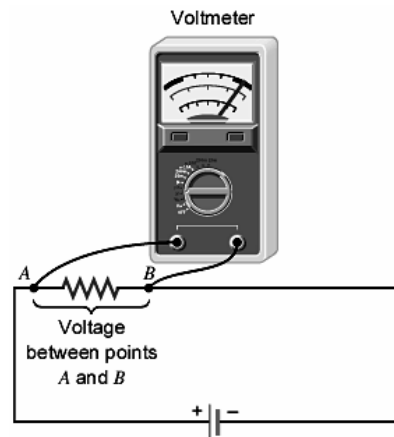

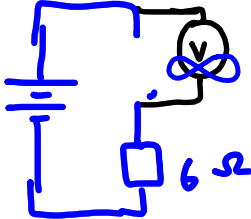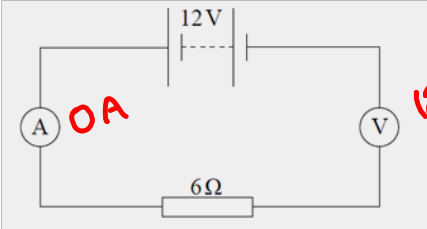
6. Which meter is improperly placed? What is the reading on each meter?



Handwritten blue notes:  $6 \Omega$ ,  $6 \Omega$ ,  $6 \Omega$ ,  $6 \Omega$ ,  $6 \Omega$ ,  $6 \Omega$


7. What is the reading on each of these non-ideal meters?

a.

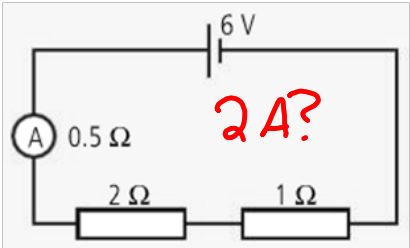

Handwritten red notes:  $2A?$ ,  $\frac{6V}{3.9\Omega} \sim 1.7A$

b.

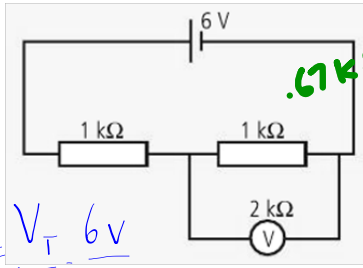

Handwritten blue notes:  $I_T = \frac{V_T}{R} = \frac{6V}{1.67k\Omega}$ ,  $3V?$

Handwritten green note:  $.67k\Omega$

