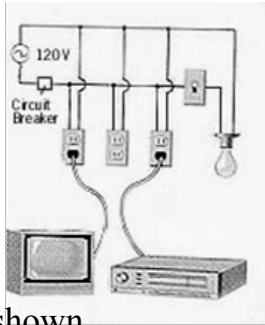



Household Wiring

1. Is most household wiring in series or in parallel? Explain.

parallel - all devices have same V



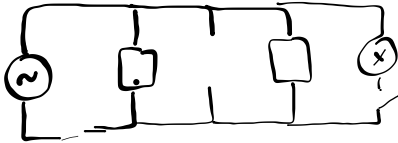2. Draw an appropriate schematic for the household circuit shown.




Household Wiring

3. What is the purpose of a fuse or a circuit breaker?

prevent too much current

How are they different?

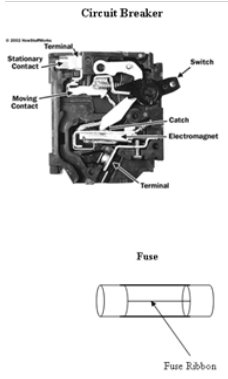fuses must be replaced
breakers can be reset



Household Wiring

4. A 900 watt toaster, a 640 watt waffle iron, and a 5 amp food processor are to be used on the same circuit. What size circuit breaker should be used?

$$P = IV$$


$$I = \frac{900W}{120V}$$

$$\frac{640W}{120V}$$

$$5A$$

Combination Circuits

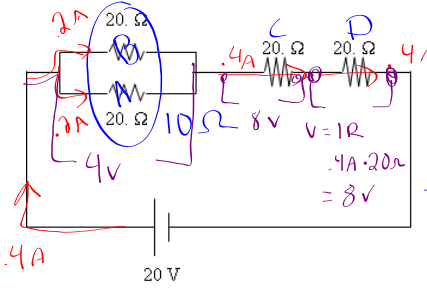
1. In each circuit below, determine the voltage drop across each resistor and the current through each resistor.



$$R_{11} = \left(\frac{1}{20\Omega} + \frac{1}{20\Omega} \right)^{-1}$$


$$R_{eq} = \left(\frac{1}{20\Omega} + \frac{1}{20\Omega} \right)^{-1} + 20\Omega + 20\Omega = 50\Omega$$
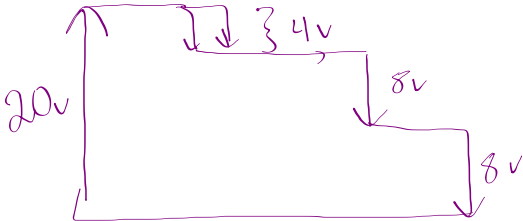
$$I_T = \frac{V_T}{R_{eq}} = \frac{20V}{50\Omega} = .4A$$




	I	V
A	.2A	4V
B	.2A	4V
C	.4A	8V
D	.4A	8V
.4A		20V

2.

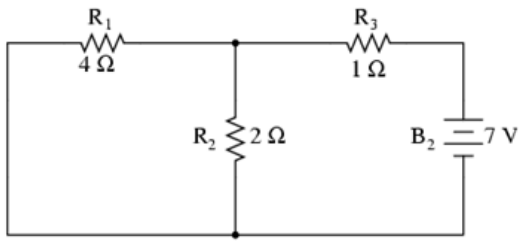

$$R_{eq} = 1\Omega + 1.3\Omega = 2.33\Omega$$
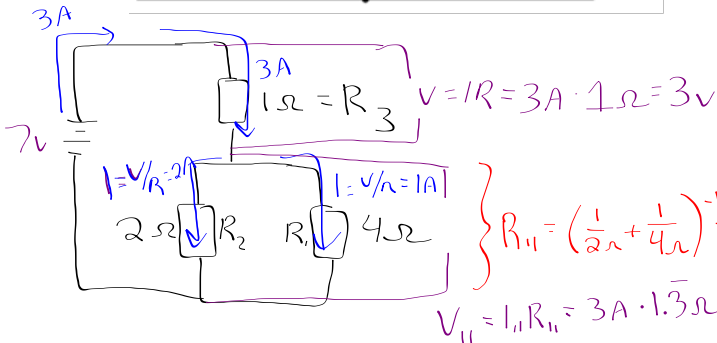
$$I_{+} = \frac{V}{R_T} = \frac{7V}{2.33\Omega} = 3A$$





	I	V
R ₁	1A	4V
R ₂	2A	4V
R ₃	3A	3V

Combination Circuits

3. Determine the current through and the voltage drop across each resistor.

$R_T = 8\Omega$
 $I_T = 3A$

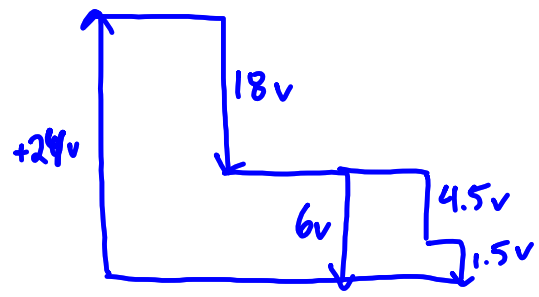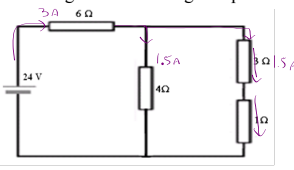

6Ω	3A	18V	P=IV ✓ . . .
4Ω	1.5A	6V	
3Ω	1.5A	4.5V	
1Ω	1.5A	1.5V	